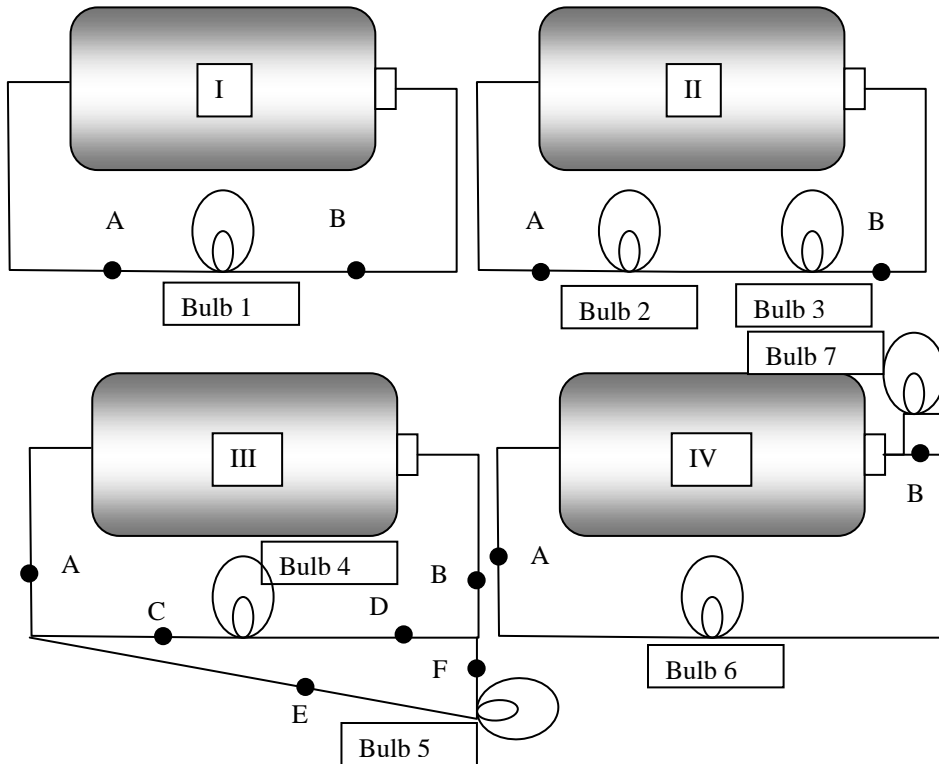


Physics 251 Prelab 4

Consider the following 4 circuits involving identical bulbs.



1) For each circuit, compare the flow of charge past point A with the flow of charge past B. Explain.

2) For circuit III, compare the currents at points A through F. Explain.

3) Rank the brightness of the bulbs. Explain.