

# Design Studio – Week 4

## Today you will:

- Evaluate and improve the RC circuit design from last week
- Design and model your own RLC circuit
- Learn about resonance and natural frequency
- Review the rubric for technical reports


## Assignments:

- Exercise worksheet for RLC circuit design and analysis
- Project 1 technical report
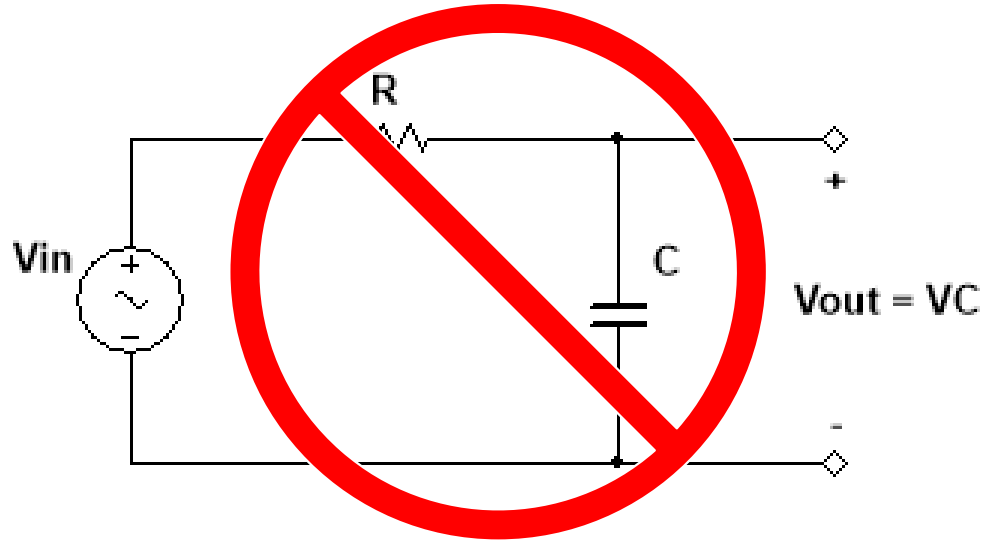
# Project 1 Review

Improve

Last week you designed, built, and tested an RC filter circuit.




**Did it work, i.e. did it meet the requirements?**

**Why not?**

# Project 1 Requirements

Ask

Recall the filter requirements:

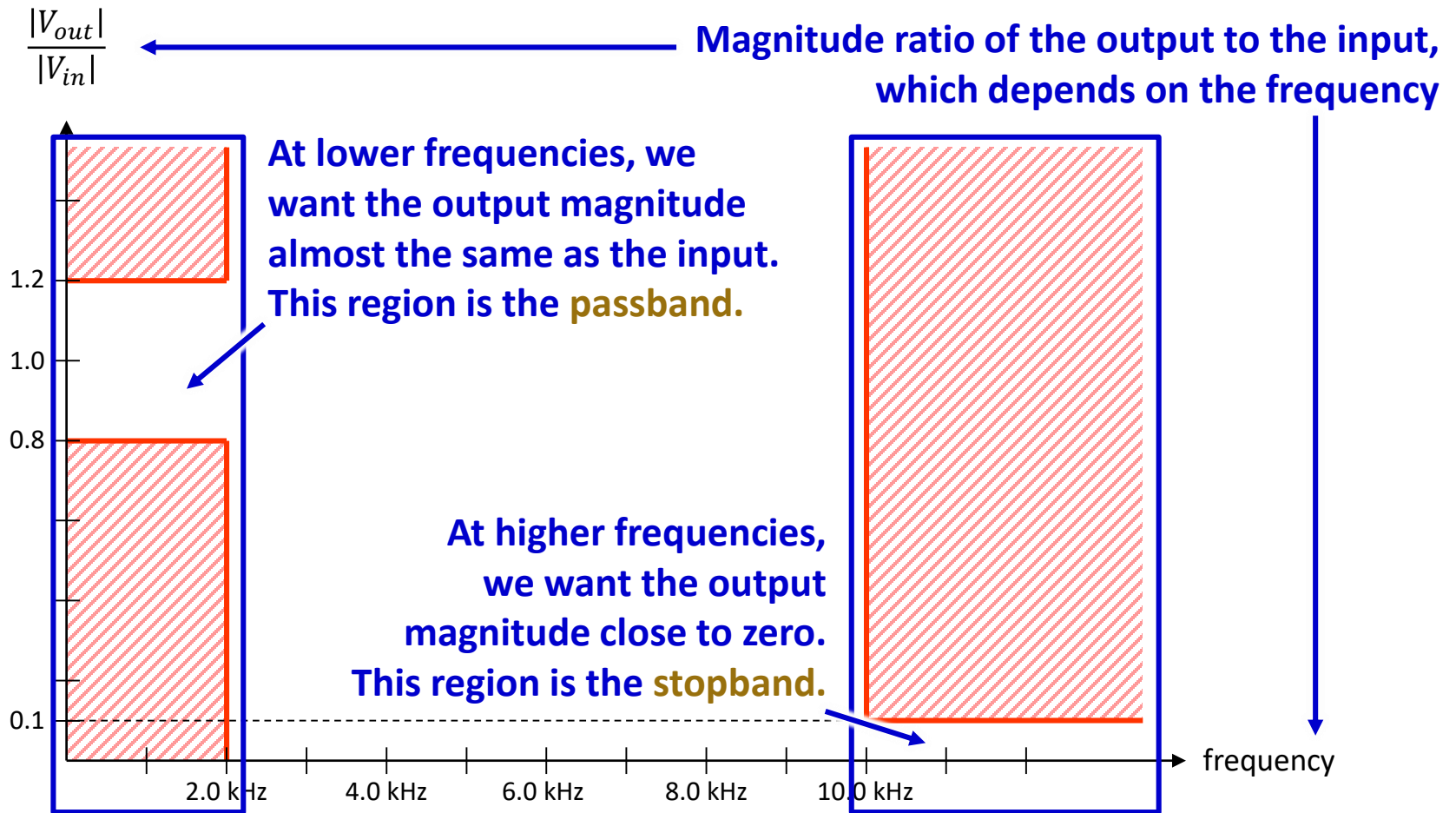


# Project 1 Redesign

Imagine

Let's see if we can improve the performance of the circuit.

Since inductors and capacitors alone with a resistor don't work, let's investigate what happens if we use both at the same time.


Using impedances:

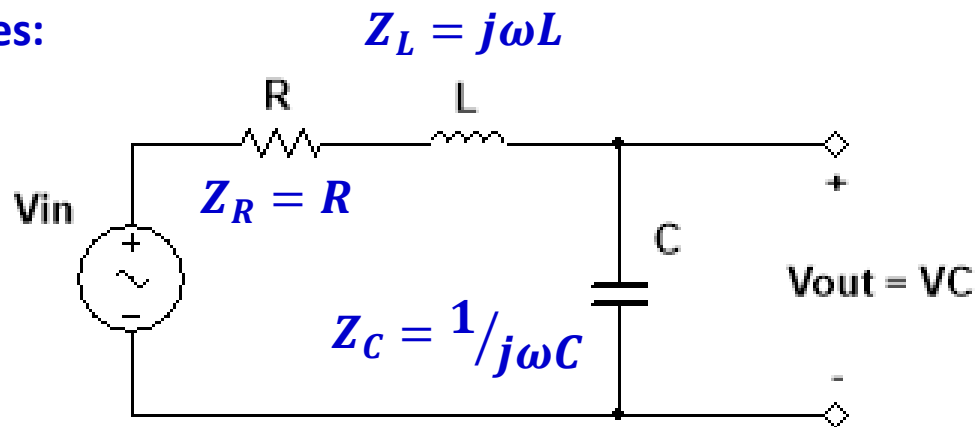

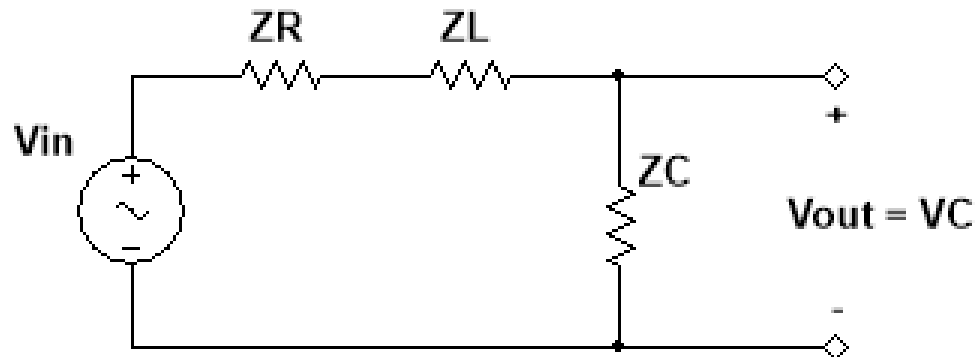
# Project 1 Redesign

Plan


How can we choose good values of L and C for our design?



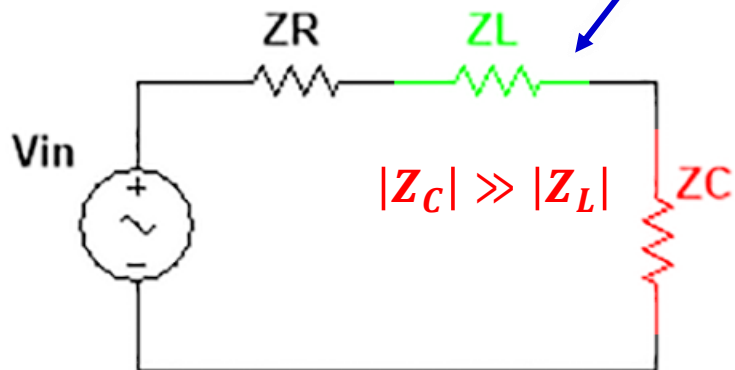At frequencies  $f \leq 2$  kHz  
(passband region)



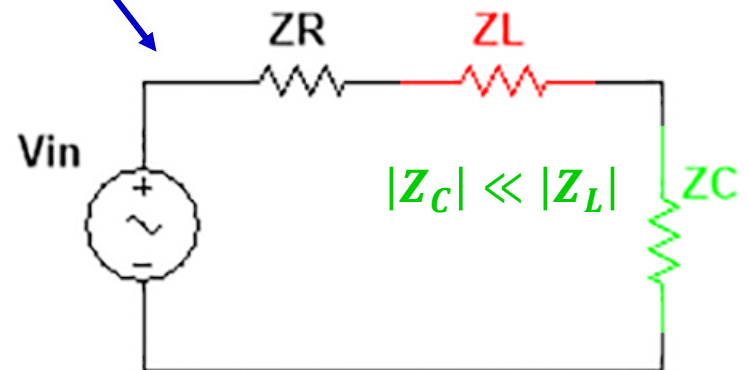
At frequencies  $f \geq 10$  kHz  
(stopband region)



We want  $|Z_C| = |Z_L|$  somewhere with  $2 \text{ kHz} < f < 10 \text{ kHz}$ .

# Concept Review – Resonance

So what happens to the inductor and capacitor when  $|Z_C| = |Z_L|$ ?

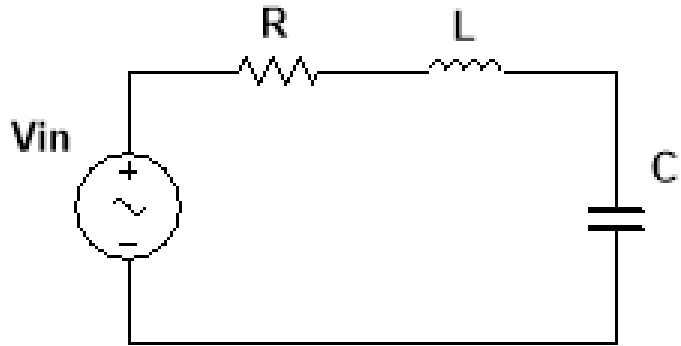


That means  $\omega L = 1/\omega C \dots$

...and  $Z_L + Z_C = j\omega L + 1/j\omega C = 0!$

So  $V_L + V_C = I(Z_L + Z_C) = 0$ , but are  $V_L = 0$  and  $V_C = 0$ ?

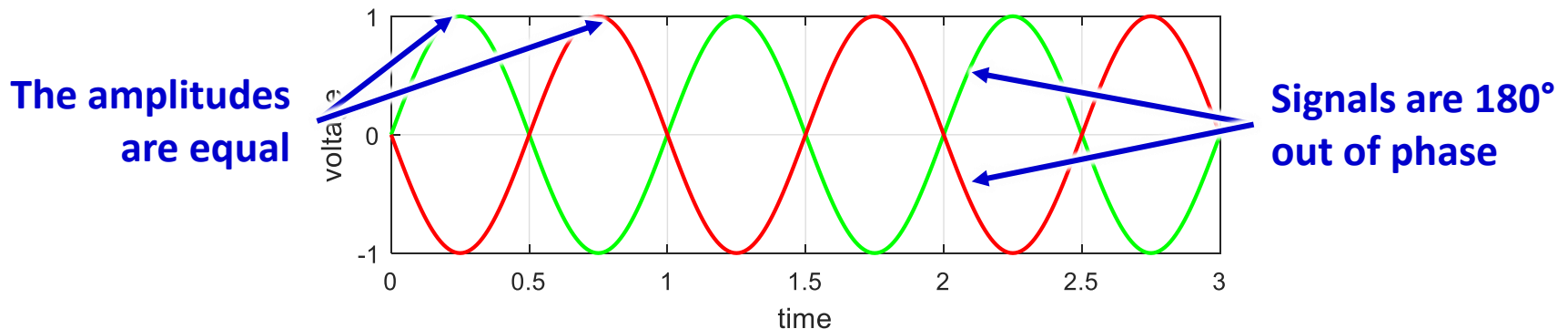No, they are just opposite of each other...



# Concept Review – Resonance

The frequency  $\omega = 1/\sqrt{LC}$  at which  $V_L + V_C = 0$  is called the resonant frequency, or the **natural frequency**.

The voltages  $V_L$  and  $V_C$  actually can become quite large in this case.

The tendency to amplify signals at the natural frequency is called **resonance**.




[Using Resonance to Break a Wine Glass](https://www.youtube.com/watch?v=BE827gwnnk4)

<https://www.youtube.com/watch?v=BE827gwnnk4>
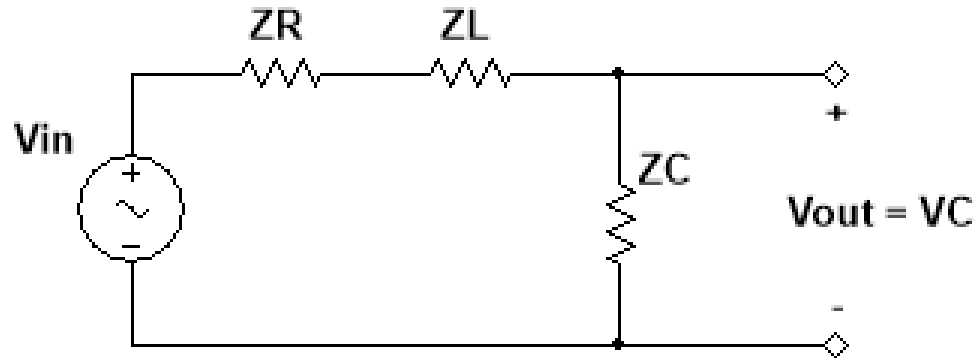
# Project 1 Redesign

Plan

How can we choose a good value of  $R$  for our design?



If  $R$  is too big,  $|Z_R| = |Z_C|$  around 2 kHz and  $V_{out} < V_{in}$ .

If  $R$  is too small,  $V_{out}$  gets very large near the natural frequency.


**Write the equations or test some values in Multisim to choose  $R$ .**


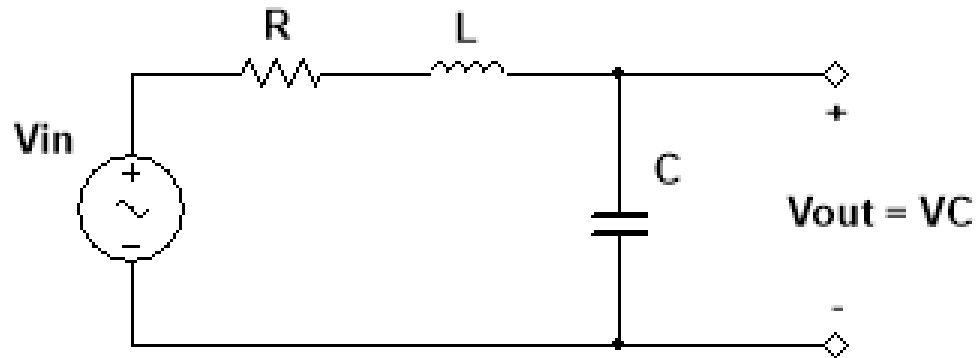
# Project 1 Modeling and Test

Create

Follow along with the worksheet to build a working version of your circuit design in Multisim with your team.



**Your instructor is here to help answer guiding questions and troubleshoot any problems that your team identifies.**

# Project 1 Technical Report

Project 1 features your first technical report. Because this is the first time you will be capturing the entire design, the report will be treated mostly as a learning opportunity.



At a top level, the report can be viewed as an account of:

- What you planned and decided (**Methods**)
- What you did and what you learned (**Results**)
- What you think you should do next (**Conclusions**)

The report should also include a cover page and references and appendices as needed.

**Let's review the rubric and example report  
posted on the Studio website.**

# Project 1 Methods

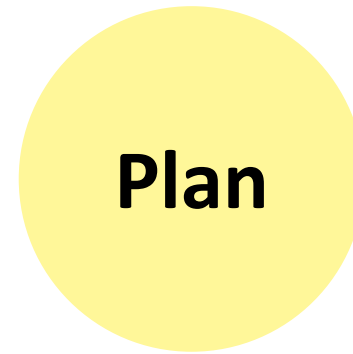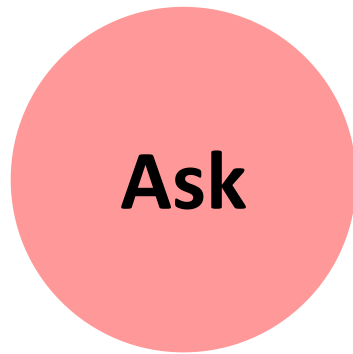

The **Methods** section covers the *Ask*, *Imagine*, and *Plan* phases.

For this project, you should include:

- The project requirements
- The RLC circuit design you are using this week
- The final values of any resistors, capacitors, and inductors

# Project 1 Results



**Create**



**Test**

The **Results** section covers the *Create* and *Test* phases.

For this project, you should include:

- The Multisim model you developed
- A table of your point measurements in Multisim
- The frequency plot of your circuit magnitude ratio from Multisim
- A check of the performance versus the requirements

# Project 1 Conclusions



The **Conclusions** section covers the *Improve* phase.

For this project, you should include (as bullet points):

- Some valuable things you learned about the circuit along the way
- *If you met the requirements*, a few steps on getting the design to the next version (e.g. prototyping, more measurements)
- *If you didn't meet the requirements*, some steps on how to go back and specifically change the design to improve it

# Project 1 Report Scope

Next week we will do some prototyping and hands on measurement of our RLC filter design.

**Your project report only needs to cover the project work and development through this week (Week 4).**

The exercises we do next week (Week 5) do not need to be included in the Project 1 report.